 


VHDL Architecture Counter example

(During this training use only the dataflow description)



Level 1:

1. Implements this model with VHDL dataflow instructions.
2. Simulate this model with $n=8$
 - a. What happens when $\text{reset}=1$ and $\text{reset}=0$
 - b. What is the minimum value and the maximum value (in hex)?
3. Implement this model with $n=26$. Assign pins CLK to 50MHz external clock, reset to a switch and $\text{out}[25]$ to a LED
 - a. What is the Led behaviour? Explain.
 - b. What is its frequency? Explain.

Level 2:

1. Modify (add the necessary hardware to) the architecture to :
 - a. create a counter which counts from 0 to N. When it reaches N it will restart to 0.
2. Draw the schematic.
3. Translate the schematic in dataflow description.
4. Simulate and validate

Level 3:

1. Modify (add the necessary hardware to) the architecture to :
 - a. create a counter which counts from 0 to N. When it reaches N it will restart to 0.
 - b. Add a signal "Enable" which lets counter runs when equal to 1 and freezes the counter when equal to 0.
2. Draw the schematic.

3. Translate the schematic in dataflow description.
4. Simulate and validate

Level 4:

1. Always in Dataflow description: One counter (Counter1) will be used to count from 0 to N. This counter increment on each rising edge of the clock. A second counter (Counter2) will be used to count from 0 to M. This counter will increment on clock rising edge AND when the Counter1 reaches N.